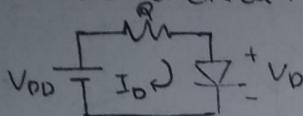


- 1) Find operating point for the diode circuit graphically using load line method.
 → Load line is constructed to determine an appropriate 'Q' point for given circuit
 In order to construct a load line Volt-Ampere characteristics of the device
 and Current expression for a given circuit.
 Let us consider a circuit as shown.



From figure,
 $V_{DD} - I_D R - V_D = 0$
 $\therefore I_D = \frac{V_{DD} - V_D}{R} \quad \text{--- (i)}$


Putting $V_D = 0$ in eqn (i) we get,

$$I_D = \text{maximum. i.e } I_{D\max} = \frac{V_{DD}}{R} \quad \text{--- (ii)}$$


Again, putting $I_D = 0$ in eqn (i)
 we get, $V_{D\max} = V_{DD} \quad \text{--- (iii)}$

Plotting eqn (ii) & (iii) in figure aside →

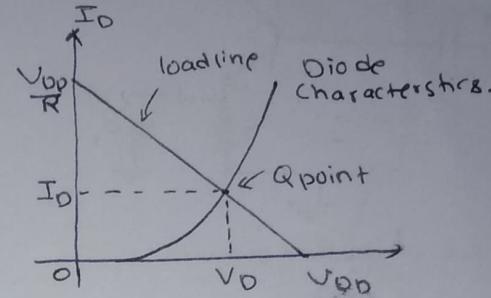Plotting these points ($V_{DD}/R, V_{DD}$) an intersection point is obtained. The point is known as O.P or Q point and gives the biasing voltage V_D & I_D .



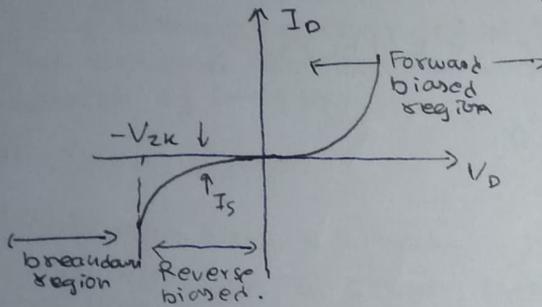- 2) Draw graphs of IV characteristics of ordinary PN junction diode and zener diode.
 Draw AC equivalent model for PN junction diode and derive its dynamic resistance.



I-V curve of PN junction diode.


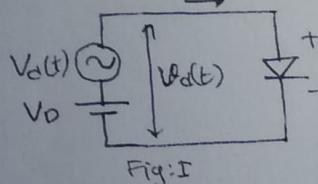


Fig: I Under small signal approximation, $V_d(t)/nV_T \ll 1$

Applying KVL
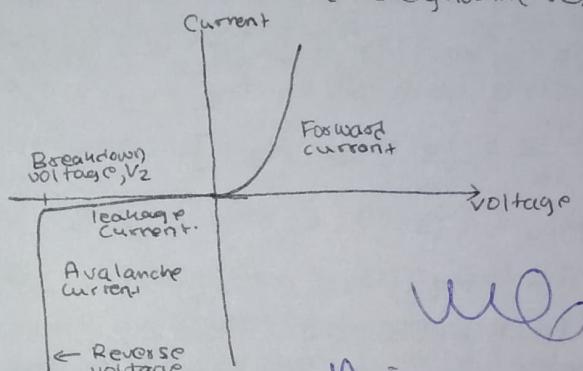
$$\begin{aligned} V_D &= V_0 + V_d(t) \\ \text{Diode current } I_D &= I_S e^{\frac{V_D}{nV_T}} = I_S e^{\frac{V_0 + V_d(t)}{nV_T}} = I_S e^{\frac{V_0}{nV_T}} \cdot e^{\frac{V_d(t)}{nV_T}} \\ &= I_D \left[1 + \frac{V_d(t)}{nV_T} + \left(\frac{V_d(t)}{nV_T} \right)^2 \frac{1}{2!} + \dots \right] \end{aligned}$$



W.L.G

$$i_D = I_D \left(1 + \frac{V_d(t)}{nV_T} \right) = I_D + i_a(t)$$


$$\text{Small signal current } i_a(t) = \frac{I_D}{nV_T} V_d(t) = \frac{V_d(t)}{r_d}$$

Where, $r_d = \frac{nV_T}{I_D}$ = dynamic resistance or AC resistance of diode.

$$\boxed{\frac{1}{i_D} \approx \frac{1}{i_d} + \frac{1}{V_d}}$$

- 3) Explain large signal model of diode.

- a) Ideal diode model.

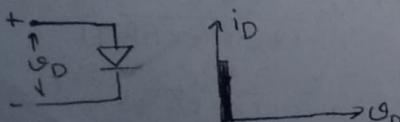


Diode eqn is

$$I_D > 0 \Rightarrow V_D = 0$$

$$I_D = 0 \Rightarrow V_D \neq 0$$


In Forward biased → Closed switch.
 In Reverse biased → Open switch.

- b) Constant voltage drop model.

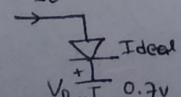

$$\begin{aligned} V_D &= 0.7V \text{ for } I_D > 0 \\ V_D &\geq 0.7V \text{ for } I_D = 0 \end{aligned}$$

- c) Piecewise linear model.

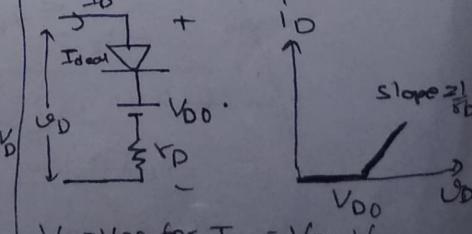

$$V_D \geq V_{D0} \text{ for } I_D = \frac{V_D - V_{D0}}{r_d}$$

* The Ebers-Moll Model:
 This model was proposed by Ebers and Moll. To determine the model of transistor, the EB junction is considered as a pn junction diode. Then normal current through the EB junction and CB junction can be determined as:

$$i_{EF} = I_{EO} \left(e^{\frac{V_{BE}}{nV_T}} - 1 \right) \quad (1)$$

Where,

i_{EF} = Forward emitter current

I_{EO} = reverse saturation Emitter current

V_{BE} = Voltage across BE junction.

V_T = Thermal voltage.

Due to emitter forward current, collector forward current i_{CF} also flows through the CB junction which can be expressed as,

$$i_{CF} = -\alpha_F i_{EF} \quad (2)$$

where, α_F is current gain

-ve sign the direction of i_{CF} w.r.t i_{EF}

Since CB junction for normal operation is reverse biased, i_{CR} flows through the CB junction.

~~$i_{CR} = I_{CO} \left(e^{\frac{V_{CB}}{nV_T}} - 1 \right) \quad (3)$~~

where, I_{CO} is the reverse saturation collector current.

Due to this reverse CC, i_{CR} some emitter reverse current i_{ER} also flows across the BE junction.

$$i_{ER} = -\alpha_R i_{CR} \quad (4)$$

From above 4 eqns,

$$i_E = i_{EF} + i_{ER} = I_{EO} \left(e^{\frac{V_{BE}}{nV_T}} - 1 \right) - \alpha_R i_{CR} \quad (5)$$

$$i_C = i_{CF} + i_{CR} = -\alpha_F i_{EF} + I_{CO} \left(e^{\frac{V_{CB}}{nV_T}} - 1 \right) \quad (6)$$

eqn (5) can be explained as parallel combination of forward biased diode with i_{EF} and $\alpha_R i_{CR}$
 eqn (6) is parallel combination of current source $\alpha_F i_{EF}$ and i_{CR}


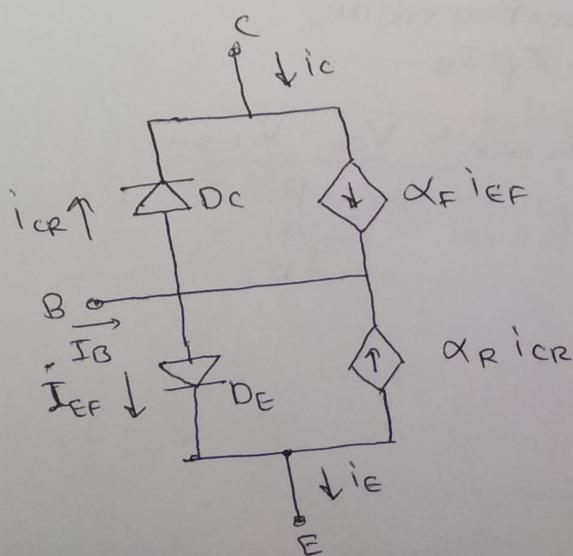
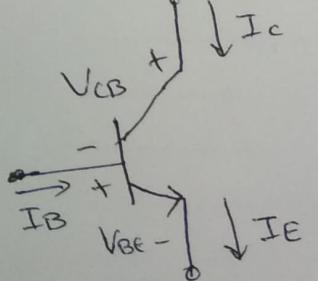


Fig: Ebers-Moll's model of transistor

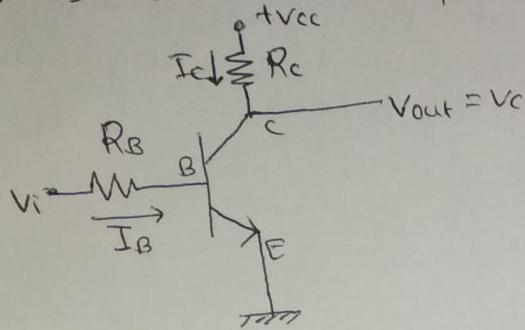* Transistor as switch - Cut off and saturation.



* Operation in cutoff mode:

- When Base-emitter junction is less than 0.7V, it will be reverse biased and practically no current flows in the transistor.

$$V_{BE} < 0.7V ; I_B = I_C = I_E = 0$$

$$\therefore V_{out} = V_c = V_{cc}$$

Since, all the currents in transistors are equal to zero, the transistor is in "OFF" condition.

* Operation in saturation mode:

- When $V_{BE} > 0.7V$, the transistor enters into active mode. The V_{BE} can be increased just by increasing the input V_i .

In active mode,

$$I_B = \frac{V_i - V_{BE}}{R_B} = \frac{V_i - 0.7}{R_B}$$

$$I_B = \frac{I_C}{\beta} \quad [\text{For active mode}]$$

Also,

$$V_c = V_{cc} - I_C R_C$$

If I_B can be increased by increasing V_i similarly I_C can be increased on increasing I_B . When I_C increases, V_c decreases. If V_c will be less than 0.7V, then C-B junction become forward biased and enters to saturation region. If V_c is further decreases, C-B junction becoming more forward biased and transistor enters into deep saturation region.

In saturation mode,

$$I_C \neq \beta I_B$$

so,

$$I_{Csat} = \frac{V_{cc} - V_{CEsat}}{R_C}$$


$$\beta_{forced} = \frac{I_{Csat}}{I_B}$$

* Crossover distortion and its elimination.

→ This distortion is the result of one of the transistor cutting off before another one starts conducting in class B amplifier.


To eliminate the error

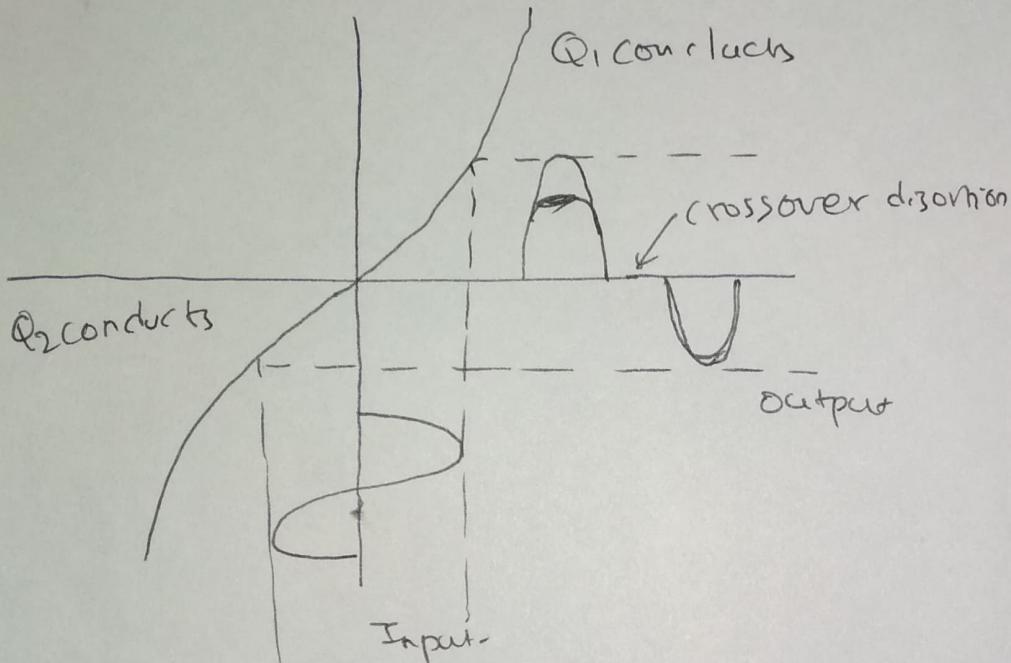It is said to be crossover distortion because it occurs during the time operation crossover from one transistor to another. To eliminate crossover distortion it is necessary to add small amount of forward bias to take two transistors to their average conduction or beyond.



* Barkhausen Criteria:


→ Block diagram of general oscillator is

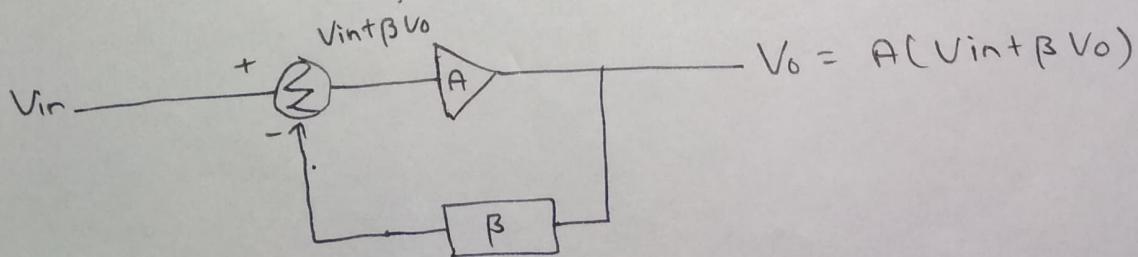

Criteria:-

- 1) Total loop gain βA should be unity ($\beta A = 1$)
- 2) Total phase difference in a loop should be zero

* Tuned Amplifier

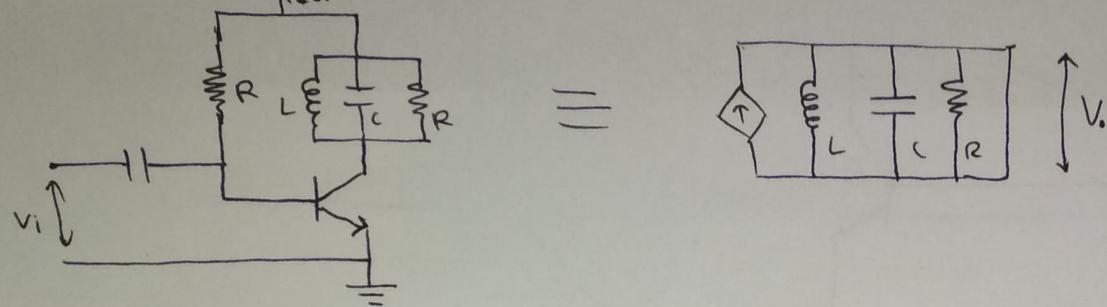

From above figure

$$V_o = I_o Z_L$$

$$\text{or } V_o = \frac{I_o}{Y_L} \quad \text{--- (1)}$$

where Y_L is the admittance of RLC

$$Y_L = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$\text{or } Y_L = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

$$\text{or } Y_L = G_L + jB \quad \text{--- (ii)}$$

At resonance frequency $B = 0$

$$\omega_0 C - \frac{1}{\omega_0 L} = 0$$

$$\text{or } \omega_0^2 = \frac{1}{LC}$$

$$\therefore \omega_0 = \frac{1}{\sqrt{LC}} \quad \text{--- (iii)}$$

At the cutoff frequency ω_c , (-3dB)

$$|B| = |G_L|$$

$$|B|^2 = |G_L|^2$$

$$\text{or } B = \pm G_L$$

$$\text{or } \omega_c C - \frac{1}{\omega_c L} = \pm \frac{1}{R} \quad \text{--- (iv)}$$

At lower Resonant frequency

$$\omega_d - \frac{1}{\omega_d L} = -\frac{1}{R} \quad \text{--- (v)}$$

At higher Resonant frequency

$$\omega_h C - \frac{1}{\omega_h L} = +\frac{1}{R} \quad \text{--- (vi)}$$


from (v) and (vi)

$$\omega_{c1} = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \quad \text{--- (A)}$$


$$\omega_{c2} = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \quad \text{--- (B)}$$

$$\text{Bandwidth } B_w = \omega_{c2} - \omega_{c1}$$


$$= \frac{1}{RC}$$

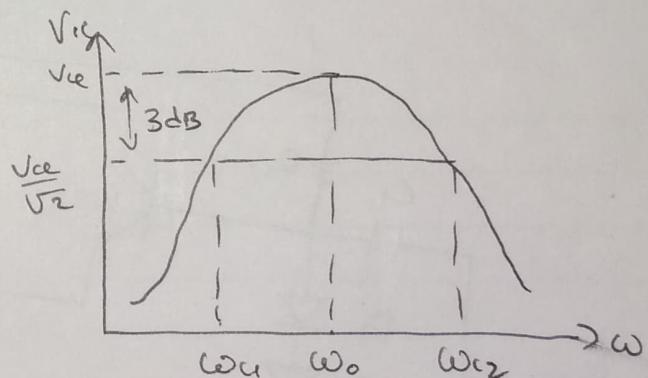

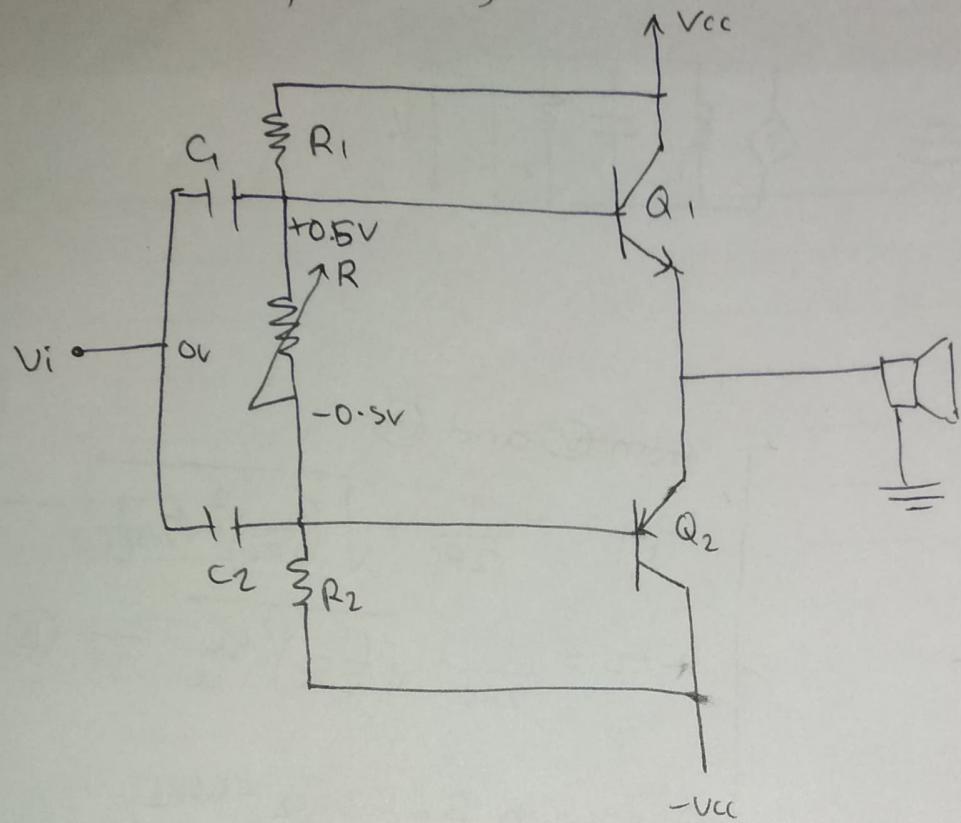
complementary symmetry of Class AB push-pull amplifier



By Darlington pair transistor

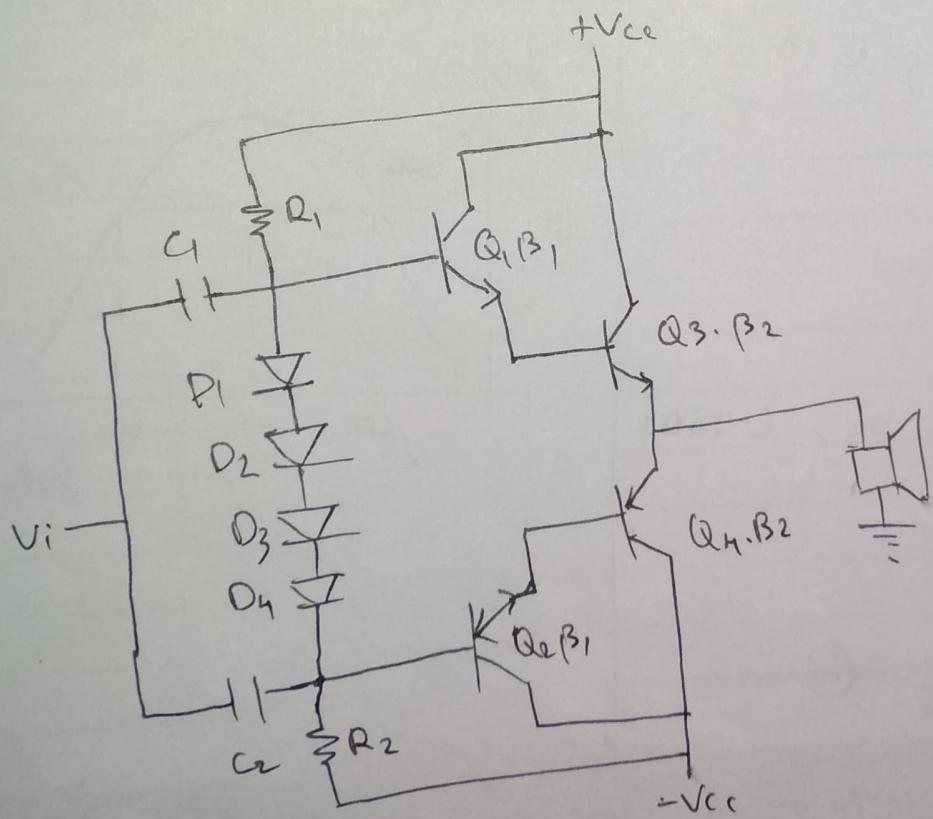

* Wein bridge Oscillator

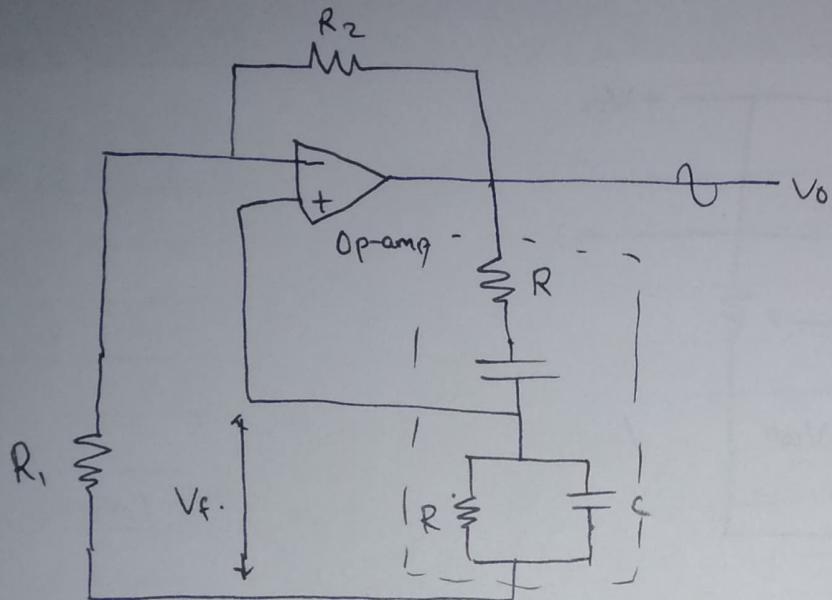

- The output of Op-Amp is fed back to both the input terminals of Op-amp through the Resistor voltage divider network and RC wein bridge circuit.
- The upper RC series and RC lower RC parallel circuit produce zero shift at frequency of oscillation.

From figure,

$$Z_1 = R + jX$$

$$Z_2 = \frac{RjX}{R + jX}$$

We have

$$V_f = V_o \frac{Z_2}{Z_1 + Z_2}$$

$$\therefore \frac{V_f}{V_o} = \frac{\frac{RjX}{R + jX}}{\frac{RjX + RjX}{R + jX}}$$

$$\therefore \frac{V_f}{V_o} = \frac{\frac{RjX}{R + jX}}{\frac{(R + jX)^2 + RjX}{(R + jX)}}$$

$$\text{or } \frac{V_f}{V_o} = \frac{RjX}{R^2 + 2RjX + j^2X^2 + RjX}$$

$$\text{or } \frac{V_f}{V_o} = \frac{RjX}{(R^2 - X^2) + 3RjX}$$

$$\text{or } \frac{V_f}{V_o} = \frac{-Rx}{j(R^2 - X^2) + 3Rx} \rightarrow 0$$

For zero shift

$$R^2 - X^2 = 0$$

$$\text{or } R^2 = X^2$$


$$\text{or } R = \frac{1}{2\pi f c}$$

$$\therefore f = \frac{1}{2\pi R C}$$

\therefore From (i)

$$\frac{V_f}{V_o} = \frac{-RjX}{-3Rx} = \frac{1}{3}$$

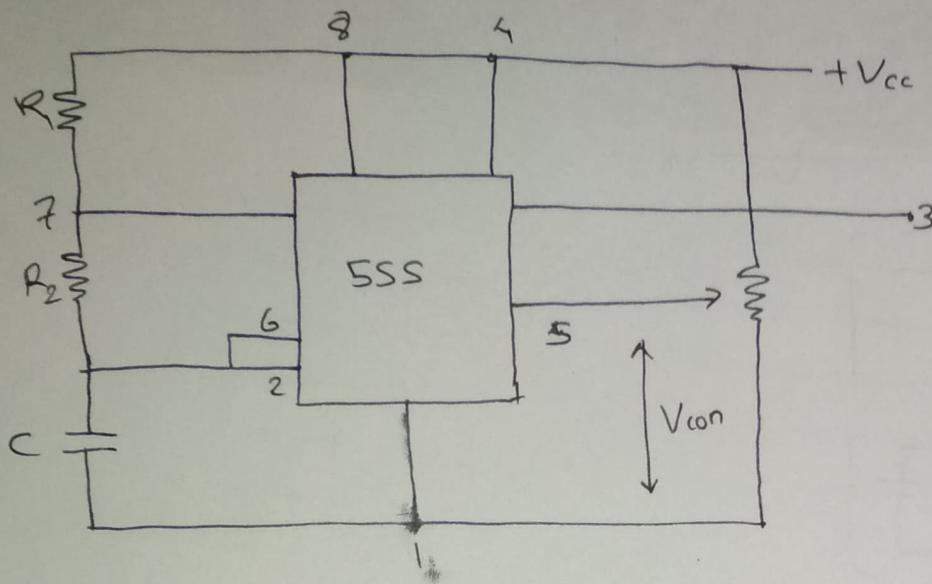* Voltage Controlled Oscillator using 555 timer



Voltage control oscillator is also called Voltage to frequency converter. The frequency can be controlled by controlling Voltage V_{con} . V_{cc} varies from $\frac{V_{con}}{2}$ to V_{con} . If we increase V_{con} , it takes capacitor longer to charge and discharge.

Let t_1 be charging time and t_2 be discharging time of capacitor,

$$V_c(t_1) = V_{\text{Applied}} - [V_{\text{Applied}} - V_{\text{initial}}] e^{-\frac{t_1}{(R_1+R_2)C}}$$

$$V_c(t_2) = V_{\text{Applied}} - [V_{\text{Applied}} - V_{\text{initial}}] e^{-\frac{t_2}{R_2C}}$$

For charging,

$$V_{con} = V_{cc} - \left[V_{cc} - \frac{V_{con}}{2} \right] e^{-\frac{t_1}{(R_1+R_2)C}}$$

$$\text{or, } \frac{t_1}{(R_1+R_2)C} = \ln \left(\frac{V_{cc} - 0.5V_{con}}{V_{cc} - V_{con}} \right)$$

For discharging,

$$V_{con} = V_{cc} - [V_{cc} - V_{con}] e^{-\frac{t_2}{R_2C}}$$

$$\text{or, } t_2 = R_2 C \ln 2$$



For time period,

$$\begin{aligned} T &= t_1 + t_2 \\ &= (R_1+R_2)C \ln \left(\frac{V_{cc} - 0.5V_{con}}{V_{cc} - V_{con}} \right) + R_2 C \ln 2 \end{aligned}$$

For frequency,

$$f = \frac{1}{T}$$

* Class A fed Amplifier:-

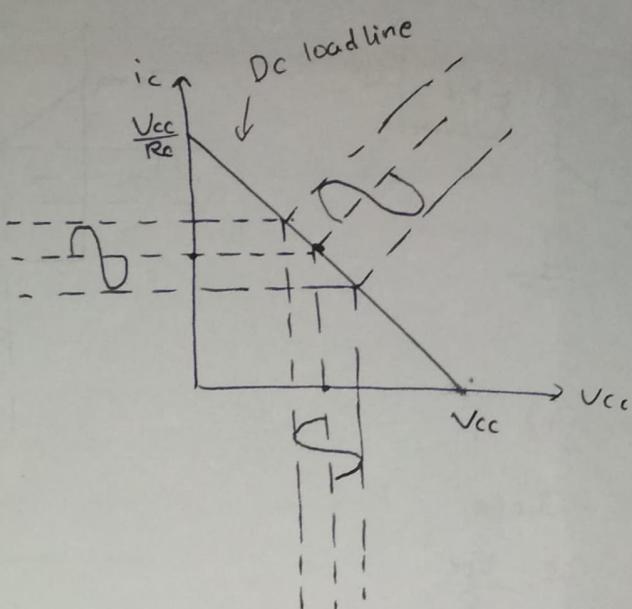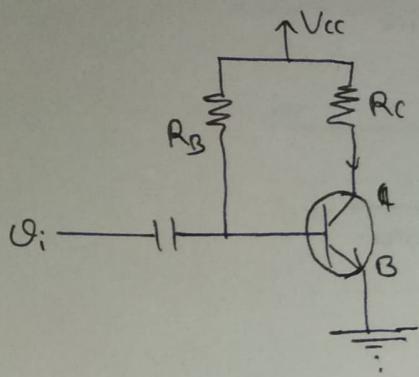

* Input power (P_i):

$$P_i = V_{CQ} I_{CQ}$$

$$= V_{CC} \cdot \frac{V_{CC}}{2R_C}$$

$$\therefore P_i = \frac{(V_{CC})^2}{2R_C}$$

* Output power (P_o):-

$$P_o = I_o V_o$$

$$= \frac{V_o}{R_C} \cdot V_o$$

$$\therefore P_o = \frac{V_o^2}{R_C}$$

$$\text{but, } V_o = \frac{V_{PP}}{2\sqrt{2}}$$

$$= \frac{V_{CC}}{2\sqrt{2}}$$

$$\therefore P_o = \frac{V_{CC}^2}{8R_C}$$



* Efficiency (η):

$$\eta = \frac{P_o}{P_i} \times 100\%$$

$$= \frac{V_{CC}^2}{8R_C} \times \frac{2R_C}{V_{CC}^2} \times 100\%$$

$$\therefore \eta_{max} = 25\%$$

* Transformer Coupled Class A Amplifier.

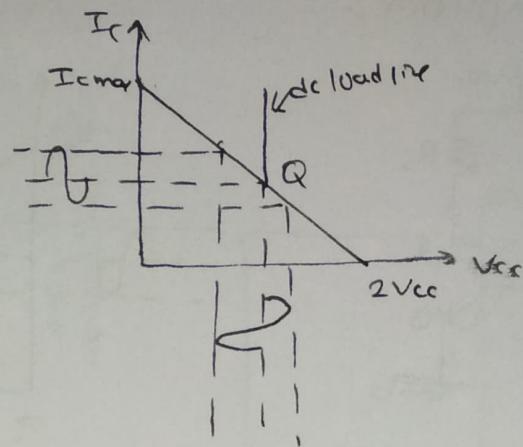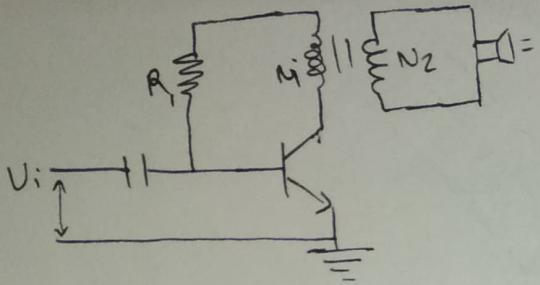

* Input Power (Pi)

$$\begin{aligned} P_i &= V_{cc} I_{cQ} \\ &= V_{cc} \cdot \frac{V_{cc}}{R} \end{aligned}$$

$$P_i = \frac{V_{cc}^2}{R} \quad \text{--- (1)}$$

where R is the resistance from primary side of transformer.

* Output Power (Po)

$$\begin{aligned} P_o &= I_o V_o \\ &= \frac{V_o^2}{R} \end{aligned}$$

where

$$V_o = \frac{V_{pp}}{2\sqrt{2}} = \frac{2V_{ce}}{2\sqrt{2}} = \frac{V_{ce}}{\sqrt{2}}$$

$$\therefore P_o = \frac{V_{ce}^2}{2R} \quad \text{--- (ii)}$$

* Efficiency:

$$\begin{aligned} \eta &= \frac{P_o}{P_i} \times 100\% \\ &= \frac{V_{ce}^2}{2R} \times \frac{R}{V_{ce}^2} \times 100\% \\ &= 50\% \end{aligned}$$


* For general efficiency.

$$\text{replace } V_{cc} = \frac{V_{ce\min} + V_{ce\max}}{2} \text{ in eqn (1)}$$

$$\& \text{ " } \quad V_{cc} = \frac{V_{ce\max} - V_{ce\min}}{2} \text{ in eqn (ii)}$$

$$\therefore \eta = 50 \left[\frac{V_{ce\max} - V_{ce\min}}{V_{ce\max} + V_{ce\min}} \right]^2 \%$$


* Hartley Oscillator

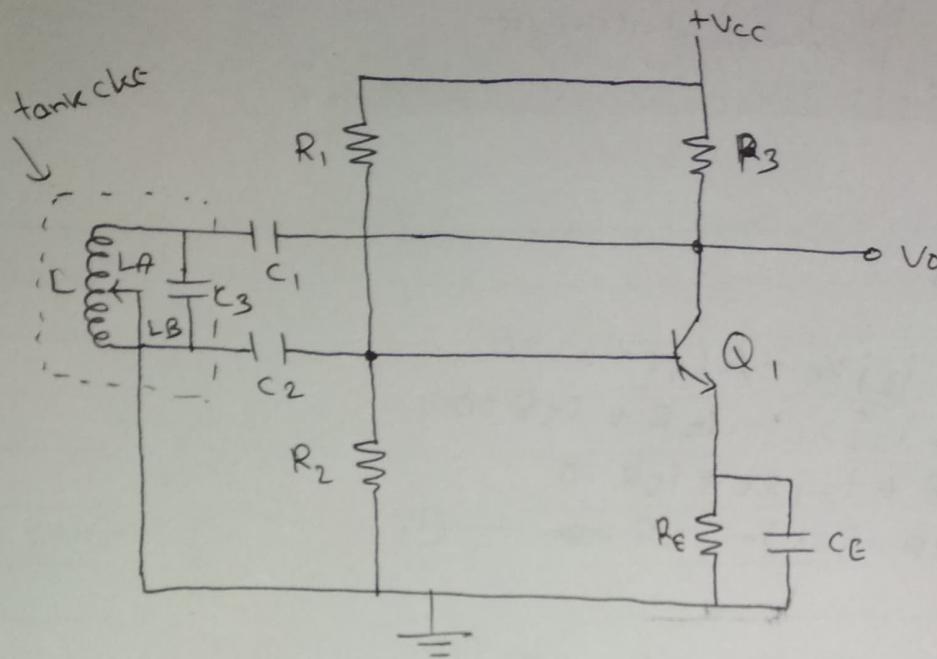

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{(LA+LB).C}}$$


* Colpitts oscillator

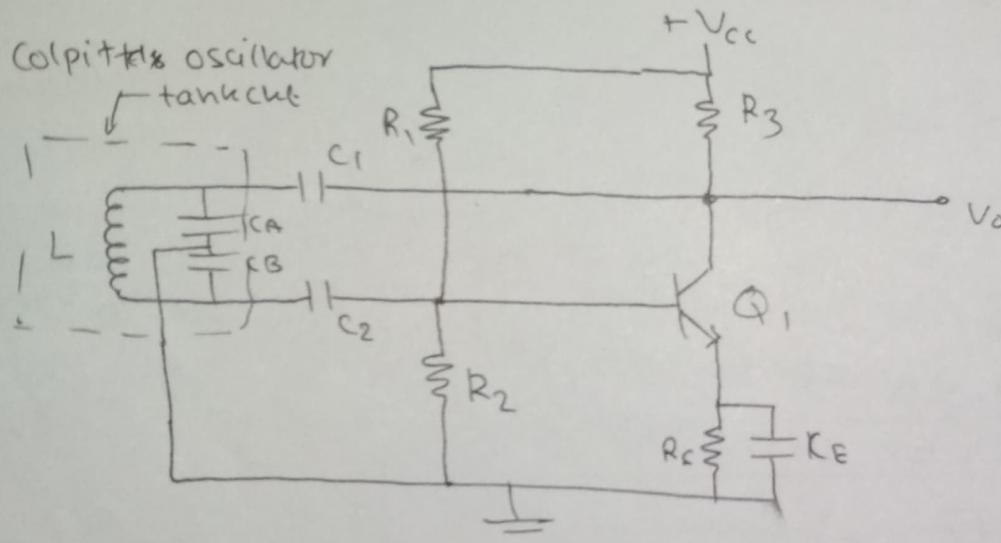


$$f = \frac{1}{2\pi\sqrt{LC}}$$

Where, $C = \frac{C_A + C_B}{C_A + C_B}$

* RC Shift oscillator

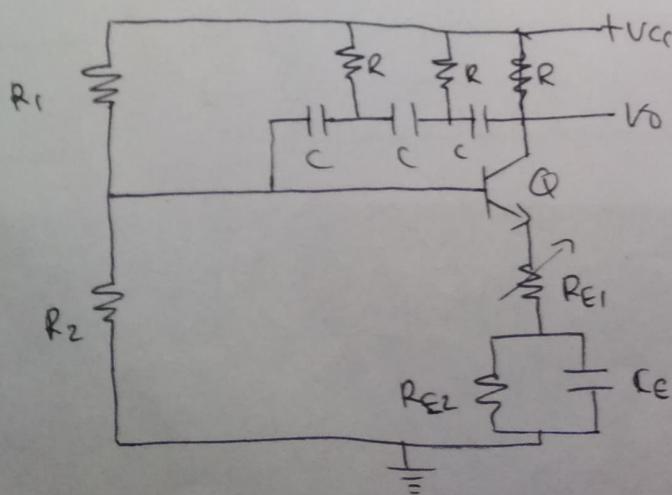

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

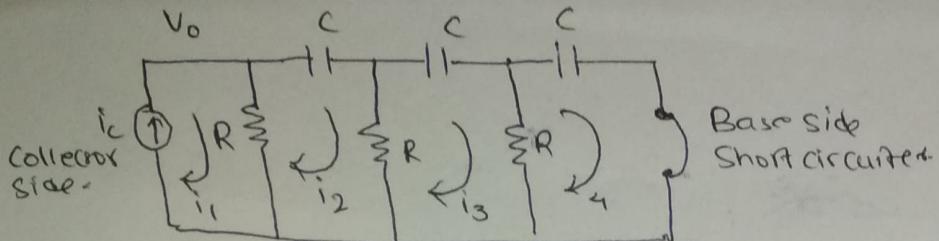

From above figure,

~~$i_1 = i_c$~~

~~$i_4 = i_b$~~

in loop ①

~~$i_1 R + R(i_2 - i_1) + i_2 j X_C - R(i_2 - i_3) = 0$~~

~~$\Rightarrow -i_2 R + i_1 R + i_2 j X_C - i_2 R + i_3 R = 0$~~

~~$\Rightarrow i_1 R - 2i_2 R + i_2 j X_C + i_3 R = 0$~~

~~$\therefore i_1 R = i_2 (2R - j X_C) - i_3 R \quad \text{--- } \textcircled{I}$~~

in loop ②

$$i_2 R = i_3 (2R - j X_C) - i_4 R \quad \text{--- } \textcircled{II}$$

in loop ③

$$i_3 R = i_4 (R - j X_C) \quad \text{--- } \textcircled{III}$$

Eliminating i_2 and i_3 from \textcircled{III} , \textcircled{II} & \textcircled{I} we get,

$$\frac{i_4}{i_1} = \frac{R^3}{R^3 - 5R^2 X^2 + j(-6R^2 X + X^3)} \quad \text{--- } \textcircled{IV}$$


For 180° phaseshift, expression containing j vanishes, i.e. $-6R^2 X + X^3 = 0$

$$X(-6R^2 + X^2) = 0 \text{ since, } X \neq 0$$

$$\therefore X = +R\sqrt{6} = \frac{1}{2\pi f_0 C}$$

$$\therefore f_0 = \frac{1}{2\pi R C \sqrt{6}}$$

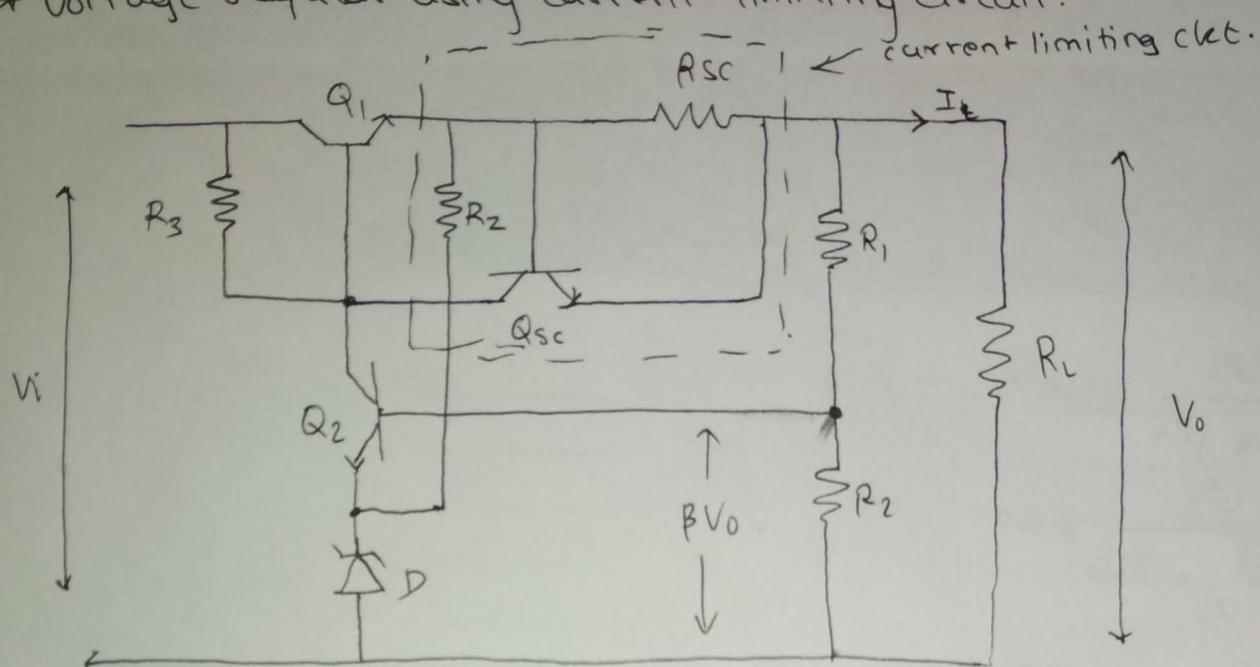* Voltage regulator using current limiting circuit.



Operation:-

- When I_L is normal, Voltage across R_{sc} is ~~normal~~ so very small so that there is no voltage on base of transistor Q_{sc} . In this moment circuit behaves as normal voltage regulator.
- When I_L is excessively increases due to short circuit or overload, Voltage across R_{sc} also increases enough to turn on the transistor Q_{sc} due to which ~~more~~ more current flows through R_3 .
- When more current flows through R_3 there lacks the ~~base~~ current in base of transistor Q_1 , due to which the conduction of Q_1 decreases preventing further increase in load current.
- In this way, the voltage and current throughout the circuit remains regulated.

We know,

- Input regulated voltage,

$$V_i = U_{R3} + U_{BE1} + V_o$$

Let $V_i = \Delta V_\phi$ & $V_o = \Delta V_o$ is very small change in dc voltages. considering AC quantities only,

$$U_i = U_{R3} + U_{BE1} + U_o$$

$$\approx U_{R3} \quad (U_{BE1} \text{ & } U_o \text{ is very small}).$$

- Output of transistor Q_2 ,

$$U_{R3} = A_v \times \beta V_o$$

$$= \frac{R_3}{R_{et} + R_2} \cdot \beta V_o \quad \left(\because A_v = \frac{R_3}{R_{et} + R_2} \right)$$

$$\approx U_i$$

Stability factor :

$$S_V = \frac{\Delta V_o}{\Delta V_i} \times 100\%$$

$$= \frac{V_o}{V_i} \times 100\%$$

$$= \frac{V_o}{A_{vB} \cdot \beta V_o} \times 100\%$$

$$= \frac{V_o}{\frac{R_3}{R_1 + R_2} \times \beta V_o} \times 100\%$$


$$= \frac{R_1 + R_2}{R_3} \times \frac{R_1 + R_2}{R_2} \times 100\%$$

$$S_V \approx 1.5\%$$

Best case, $S_V = 0$

worst case, $S_V = 1$

* AMV using 555 timer

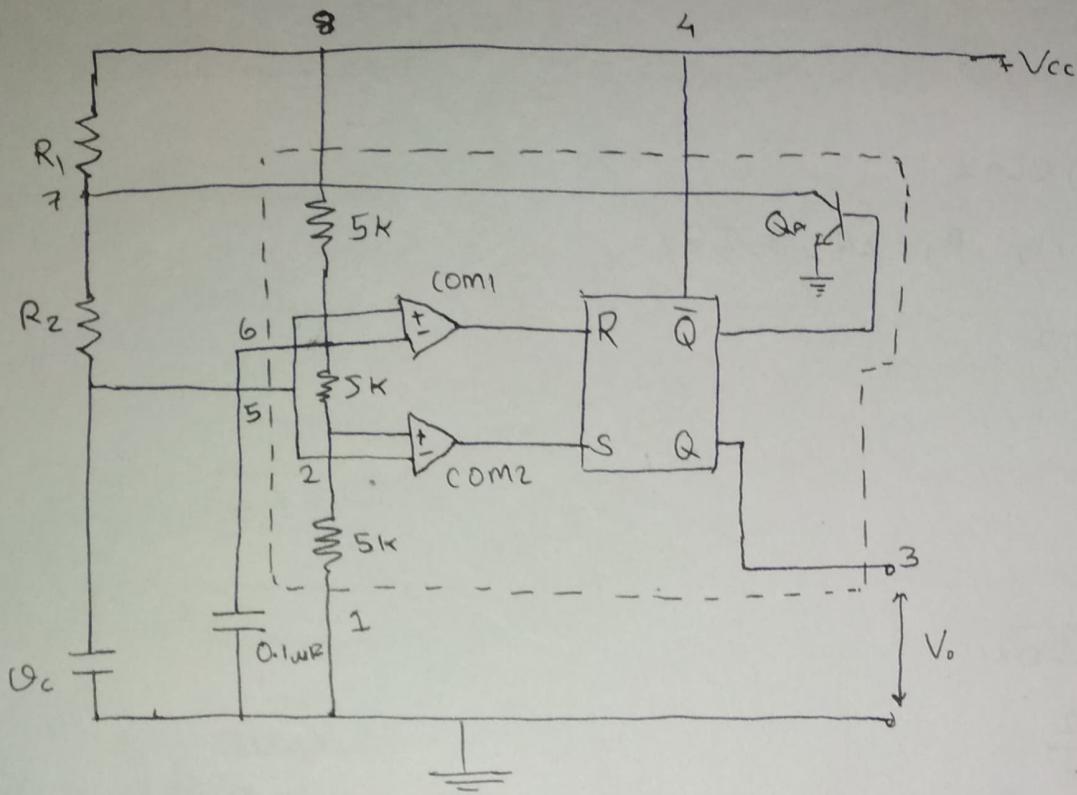

Operation:

- When $V_c = 0$, $R = 0$ & $S = 1$, $Q = 1$ and $\bar{Q} = 0$, Q_A transistor turns off, pin 7 is open circuited, capacitor starts to charge through $(R_1 + R_2)$ towards V_{cc} .
- When $V_c > \frac{V_{cc}}{3}$, $R = 0$ & $S = 0$, no charge, Q_A still turns off so capacitor charging continues.
- When $V_c > \frac{2V_{cc}}{3}$, $R = 1$ & $S = 0$, $Q = 0$, $\bar{Q} = 1$, Q_A transistor turns on, pin 7 is short circuited to ground. so capacitor starts to discharge through R_2 towards ground. from $\frac{2V_{cc}}{3}$
- When $V_c < \frac{2V_{cc}}{3}$, $R = 0$ & $S = 0$, no charge, capacitor continues discharging
- When $V_c \leq \frac{V_{cc}}{3}$, $R = 0$ & $S = 1$, $Q = 1$ & $\bar{Q} = 0$, Q_A transistor turns off and capacitor starts to charge again.
- Whole process repeated endlessly

For Time period & frequency,

→ For charge
Let t_1 be the charging time & t_2 be the discharging time
of capacitor.

$$V_c(t_1) = V_{\text{Applied}} - (V_{\text{Applied}} - V_{\text{Initial}}) e^{-\frac{t_1}{(R_1+R_2)C}}$$

$$V_c(t_2) = V_{\text{Applied}} - (V_{\text{Applied}} - V_{\text{Initial}}) e^{-\frac{t_2}{R_2C}}$$

For charging,

$$t_1 = (R_1 + R_2) C \ln 2$$

For discharging,

$$t_2 = R_2 C \ln 2$$

$$T = t_1 + t_2$$

$$\therefore T = (R_1 + 2R_2) C \ln 2$$

when, $2R_2 \gg R_1$, $R_1 + 2R_2 \approx 2R_2$



$$\therefore T = 2R_2 C \ln 2$$

For frequency,

$$\begin{aligned} f &= \frac{1}{T} \\ &= \frac{1}{2R_2 C \ln 2} \end{aligned}$$

$$\therefore f = \frac{0.72}{RC}$$

* Class B push-pull amplifier

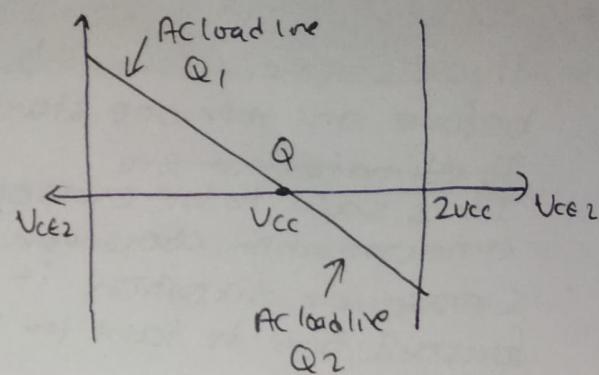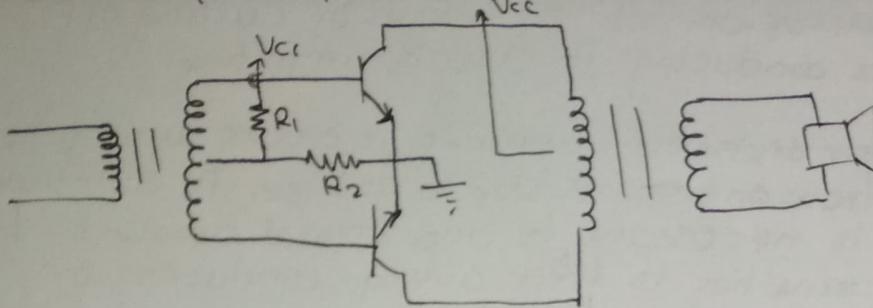

* Input power:

$$\begin{aligned} P_i &= V_{cc} I_{dc} \\ &= V_{cc} \cdot \frac{2}{\pi} \frac{V_{cc}}{R} \\ &= \frac{2}{\pi} \frac{V_{cc}^2}{R} \end{aligned}$$

* Output power:

$$\begin{aligned} P_o &= I_o V_o \\ &= \frac{V_o}{R} \cdot V_o \\ &= \frac{V_o^2}{R} \end{aligned}$$



$$\text{But, } V_o = \frac{V_{pp}}{2\sqrt{2}} = \frac{2V_{cc}}{2\sqrt{2}} = \frac{V_{cc}}{\sqrt{2}}$$

$$\therefore P_o = \frac{V_{cc}^2}{2R}$$

* Efficiency:

$$\begin{aligned} \eta &= \frac{P_o}{P_i} \times 100\% \\ &= \frac{V_{cc}^2}{2R} \cdot \frac{\pi}{2} \frac{R}{V_{cc}^2} \times 100\% \\ &= \frac{25\pi}{4} \\ \therefore \eta &= 78.5\% \quad (\text{max efficiency}) \end{aligned}$$

* Transformer Coupled Class A Amplifier.

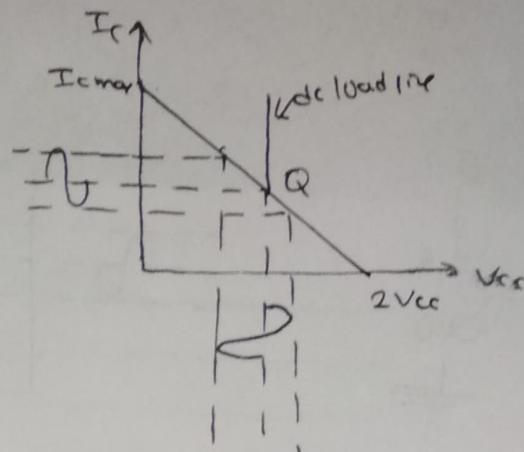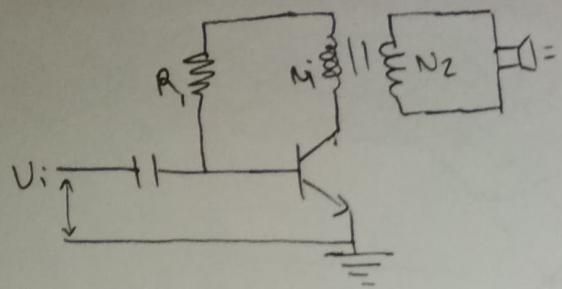

* Input Power (P_i)

$$P_i = V_{cc} I_{cEQ}$$

$$= V_{cc} \cdot \frac{V_{cc}}{R}$$

$$P_i = \frac{V_{cc}^2}{R} \quad \text{--- (1)}$$

where R is the resistance from primary side of transformer.

* Output Power (P_o)

$$P_o = I_o V_o$$

$$= \frac{V_o^2}{R}$$

where

$$V_o = \frac{V_{pp}}{2\sqrt{2}} = \frac{2V_{ce}}{2\sqrt{2}} = \frac{V_{ce}}{\sqrt{2}}$$

$$\therefore P_o = \frac{V_{ce}^2}{2R} \quad \text{--- (11)}$$

* Efficiency:

$$\eta = \frac{P_o}{P_i} \times 100\%$$

$$= \frac{V_{cc}^2}{2R} \times \frac{R}{V_{ce}^2} \times 100$$

$$= 50\%$$



* For general efficiency:

$$\text{replace } V_{cc} = \frac{V_{ce\min} + V_{ce\max}}{2} \text{ in eqn (1)}$$

$$\& \text{ " } \quad V_{cc} = \frac{V_{ce\max} - V_{ce\min}}{2} \text{ in eqn (11)}$$

$$\therefore \eta = 50 \left[\frac{V_{ce\max} - V_{ce\min}}{V_{ce\max} + V_{ce\min}} \right]^2 \%$$

* Class A fed Amplifier:-

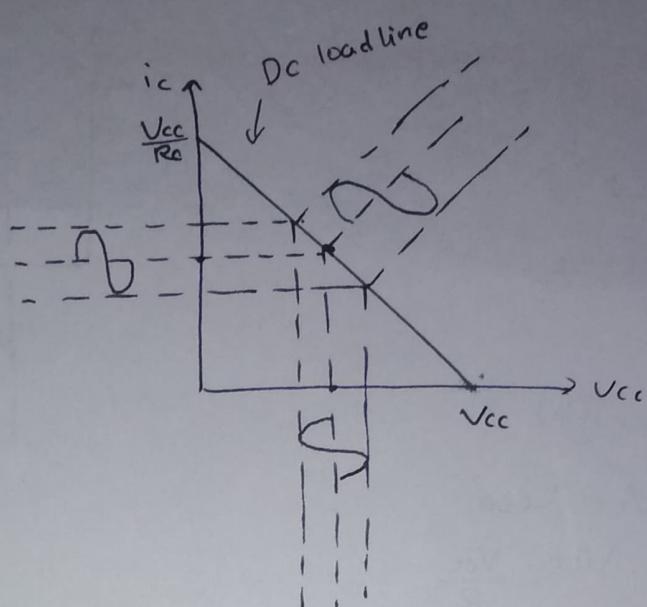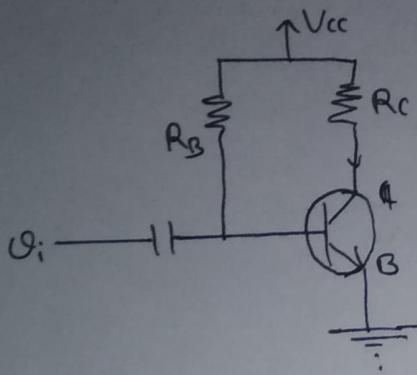

* Input power (P_i):

$$\begin{aligned} P_i &= V_{ce} I_{cq} \\ &= V_{cc} \cdot \frac{V_{cc}}{2R_c} \\ \therefore P_i &= \frac{(V_{cc})^2}{2R_c} \end{aligned}$$

* Output power (P_o):-

$$\begin{aligned} P_o &= I_o V_o \\ &= \frac{V_o}{R_c} \cdot V_o \\ \therefore P_o &= \frac{V_o^2}{R_c} \end{aligned}$$

$$\begin{aligned} \text{but, } V_o &= \frac{V_{pp}}{2\sqrt{2}} \\ &= \frac{V_{cc}}{2\sqrt{2}} \\ \therefore P_o &= \frac{V_{cc}^2}{8R_c} \end{aligned}$$


* Efficiency (η):

$$\begin{aligned} \eta &= \frac{P_o}{P_i} \times 100\% \\ &= \frac{V_{cc}^2}{8R_c} \times \frac{2R_c}{V_{cc}^2} \times 100\% \end{aligned}$$

$$\therefore \eta_{max} = 25\%$$

* Precision Rectifier Circuit:

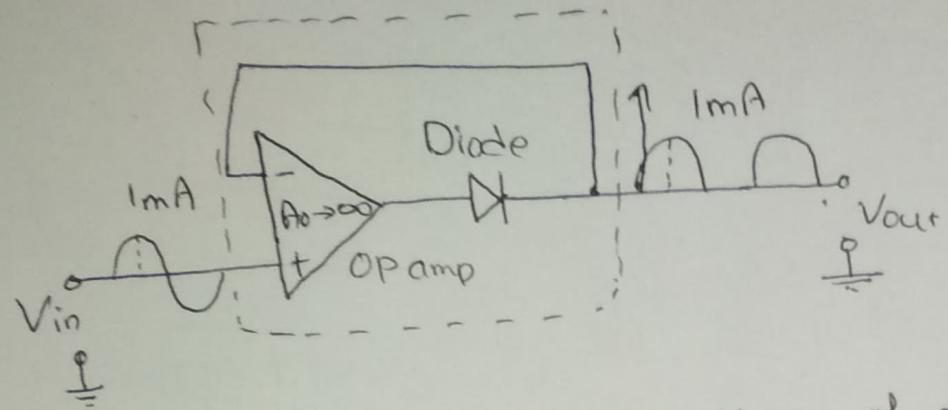→ It is a special class of wave shaping circuit used in design of instrumentation systems with very precise transfer characteristics.



- For positive input cycle output voltage of opamp will go higher positive and diode will conduct establishing closed feedback path b/w Opamp output and negative input terminal. This will cause a virtual short circuit to appear b/w two input terminals of opamp.

$$V_{out} = V_{in} \text{ for } V_{in} \geq 0$$

- For opamp to start operation, V_{in} has to exceed only a negligible small voltage equal to diode drop divided by opamp's open-loop gain.

